

## Marking Scheme

| Question number | Answer   | Notes  | Marks  |
|-----------------|--|--|--------|
| 1 (a) (i)       | A  |  | 1      |
| (ii)            | B  |  | 1      |
| (b) (i)         | C  |  | 1      |
| (ii)            | nearest above (DOP)  |  | 1      |
| (iii)           | Comment on device –<br>(plastic) insulator / does not conduct; | (double) insulated / no current (through) / cannot become live | 1<br>1 |
|                 | Comment on user –<br>no risk of shock / electrocution;         | No electricity reaches user / person cannot touch live parts   |        |

| Question number | Answer   | Notes  | Marks |
|-----------------|--|--|-------|
| 2 (a) (i)       | voltage = current x resistance   | ACCEPT equivalent rearrangement<br>ACCEPT suitable abbreviations e.g. $V = I \times R$<br>REJECT $V = I \times \square$<br>REJECT equation 'triangles' alone   | 1     |
| (ii)            | 1.2 x 4.0;<br>4.8 (V);   |  | 2     |
| (iii)           | 12 – 4.8;<br>7.2 (V);  | ECF on (ii)  | 2     |
| (iv)            | $E = VI$ (NO MARK)<br>time conversion to seconds (5.0 x 60);<br>7.2 x 1.2 x (5.0 x 60);<br>2600 (J); | ECF on (iii)   | 3     |
| (v)             | idea of energy losses<br><br>rate of energy loss = rate of energy supply (at steady temp)            | Allow 2592 or 2590<br>ALLOW 2500/2520 (J) for full marks (using 7 V)<br>ALLOW 42 (J) or 43.2 (J) for 2 marks (using 5 mins)<br><br>NB this statement alone scores (2) as it includes idea of energy loss | 2     |

| Question number | Answer  | Notes   | Marks |
|-----------------|---|---|-------|
| 2 (b) (i)       | X – series,<br>Y – parallel   | BOTH REQUIRED for the mark  | 1     |
| (ii)            | THREE SUITABLE, e.g.-<br><br>series advantage – fewer wires;<br>series advantage – lower resistance values;<br>series disadvantage – one fails, circuit fails;<br>series disadvantage – no independent control; | ALLOW REVERSE ARGUMENTS in terms of parallel circuits but do not award the same mark twice<br><br>IGNORE refs to efficiency<br>ACCEPT correct answers that link to battery voltage / current, etc | Max 3 |